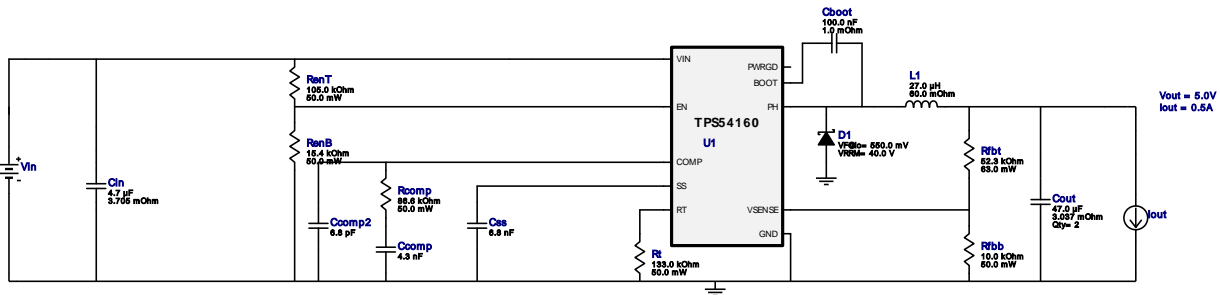






WEBENCH® Design Report





Design : 5 TPS54160DGQR
TPS54160DGQR 10.8V-13.2V to 5.00V @ 0.5A















Electrical BOM



Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cboot	MuRata	GRM155R71A104KA01D Series= X7R	Cap= 100.0 nF ESR= 1.0 mOhm VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	0402 3 mm ²
Ccomp	Kemet	C0603C432J5GAC7867 Series= C0G/NP0	Cap= 4.3 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.09	0603 5 mm ²
Ccomp2	AVX	06031U6R8BAT2A Series= C0G/NP0	Cap= 6.8 pF VDC= 100.0 V IRMS= 0.0 A	1	\$0.07	0603 5 mm ²
Cin	MuRata	GRM31CR71E475KA88L Series= X7R	Cap= 4.7 uF ESR= 3.705 mOhm VDC= 25.0 V IRMS= 2.8649 A	1	\$0.08	1206_190 11 mm ²
Cout	MuRata	GRM32ER61C476KE15L Series= X5R	Cap= 47.0 uF ESR= 3.037 mOhm VDC= 16.0 V IRMS= 4.59346 A	2	\$0.38	1210_280 15 mm ²
Css	TDK	C2012C0G1H682J060AA Series= C0G/NP0	Cap= 6.8 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.04	0805 7 mm ²
D1	Fairchild Semiconductor	SS14FL	VF@Io= 550.0 mV VRRM= 40.0 V	1	\$0.04	SOD-123F 12 mm ²
L1	Bourns	SDR1307-270ML	L= 27.0 uH 60.0 mOhm	1	\$0.42	SDR1307 226 mm ²
Rcomp	Yageo	RC0201FR-0786K6L Series= ?	Res= 86.6 kOhm Power= 50.0 mW Tolerance= 1.0%	1	\$0.01	0201 2 mm ²
RenB	Yageo	RC0201FR-0715K4L Series= ?	Res= 15.4 kOhm Power= 50.0 mW Tolerance= 1.0%	1	\$0.01	0201 2 mm ²
RenT	Yageo	RC0201FR-07105KL Series= ?	Res= 105.0 kOhm Power= 50.0 mW Tolerance= 1.0%	1	\$0.01	0201 2 mm ²

Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Rfbb	Yageo	RC0201FR-0710KL Series= ?	Res= 10.0 kOhm Power= 50.0 mW Tolerance= 1.0%	1	\$0.01	 0201 2 mm ²
Rfbt	Vishay-Dale	CRCW040252K3FKED Series= CRCW...e3	Res= 52.3 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
Rt	Yageo	RC0201FR-07133KL Series= ?	Res= 133.0 kOhm Power= 50.0 mW Tolerance= 1.0%	1	\$0.01	 0201 2 mm ²
U1	Texas Instruments	TPS54160DGQR	Switcher	1	\$1.19	 S-PDSO-G10 24 mm ²

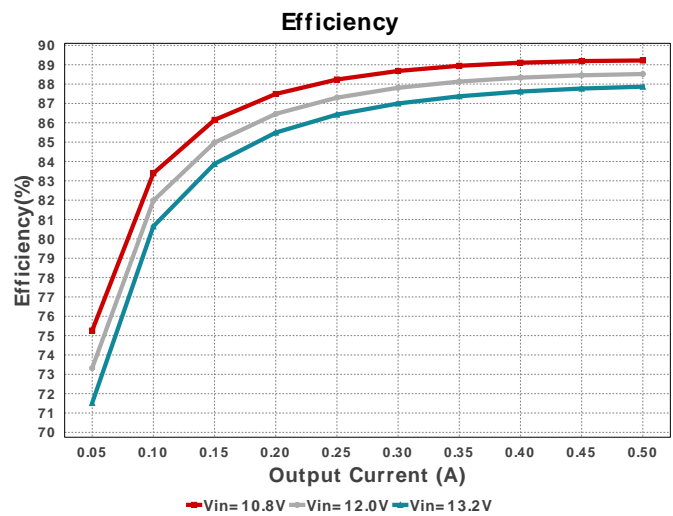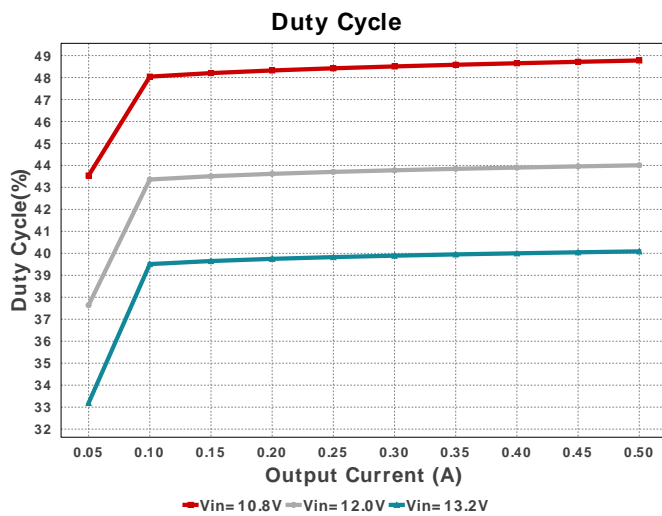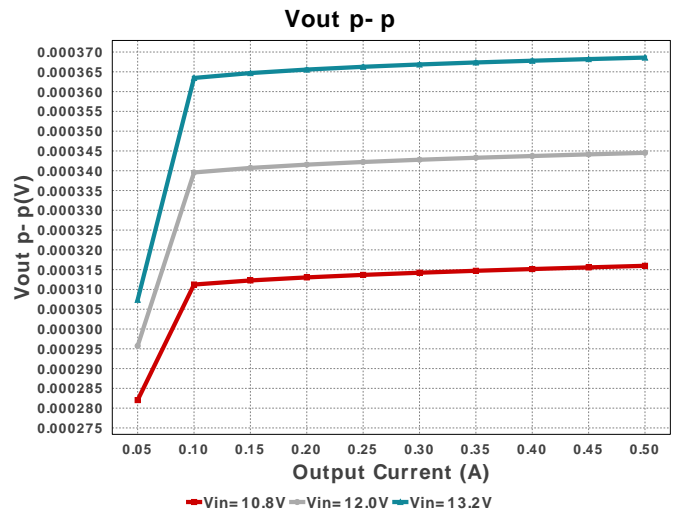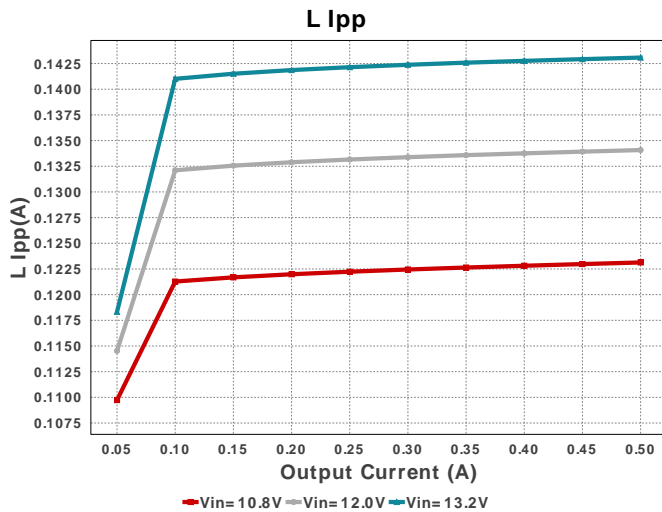

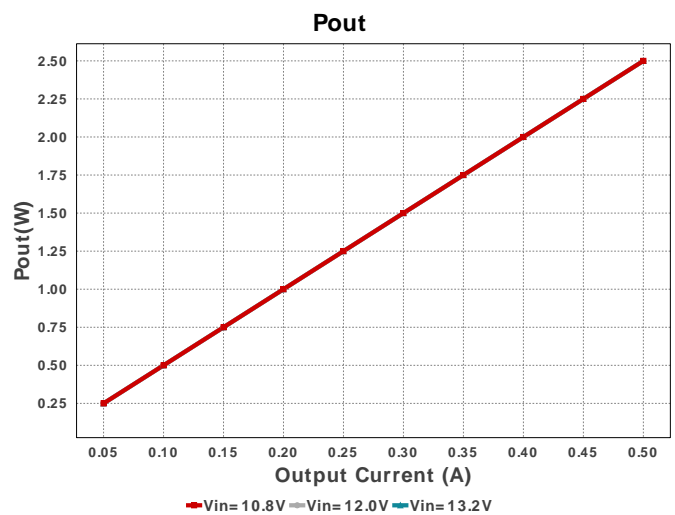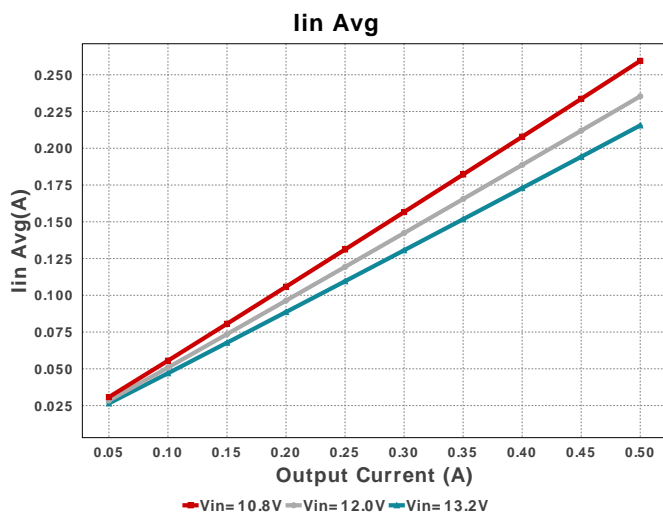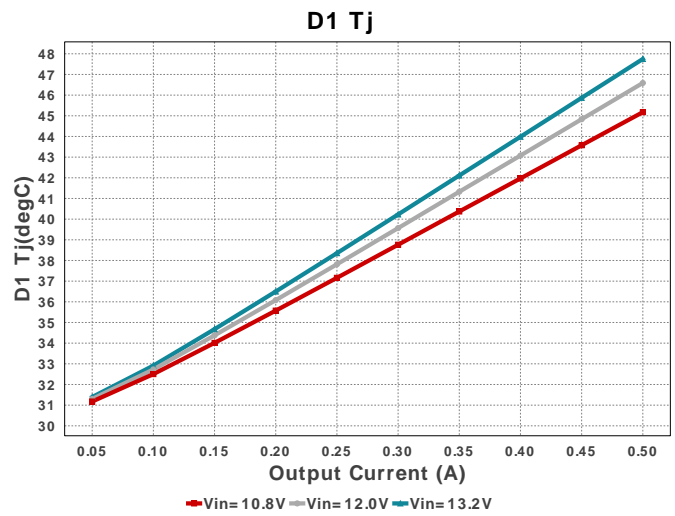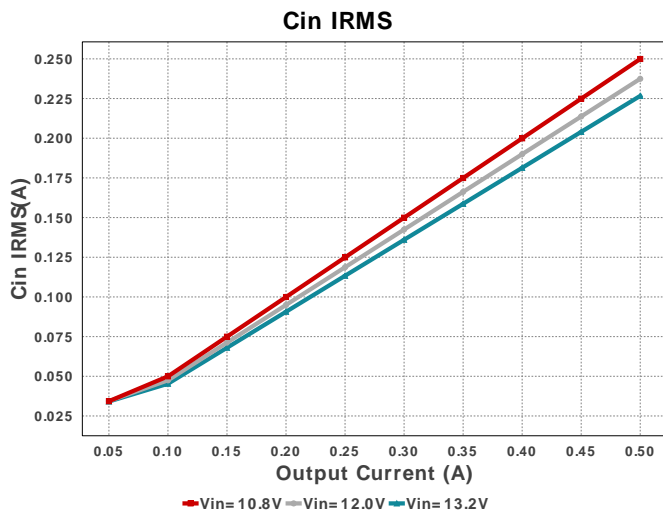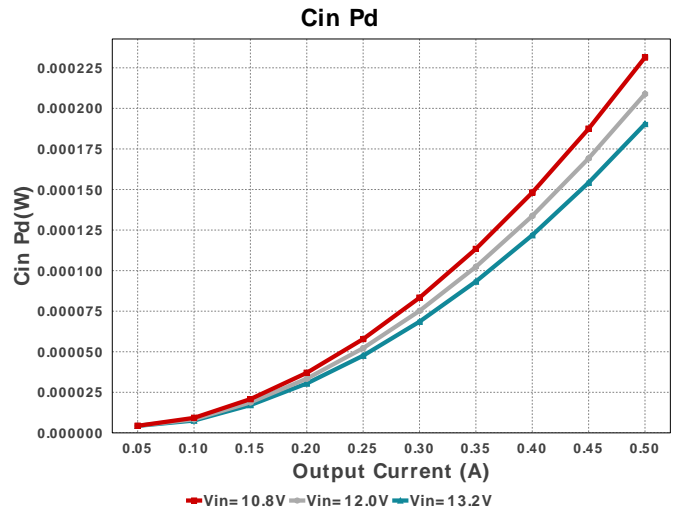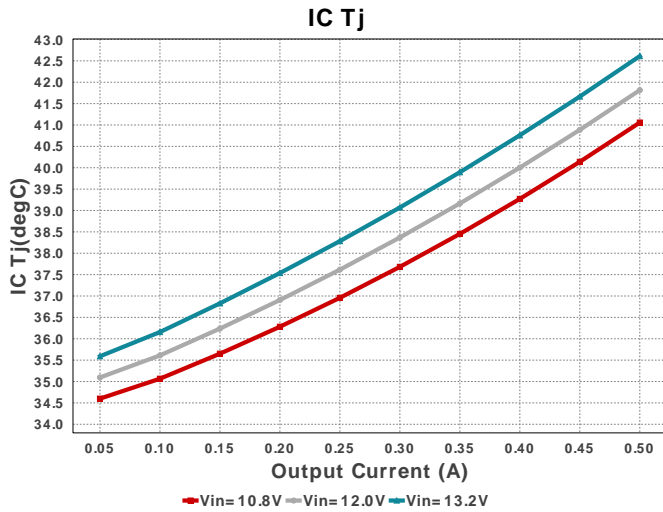

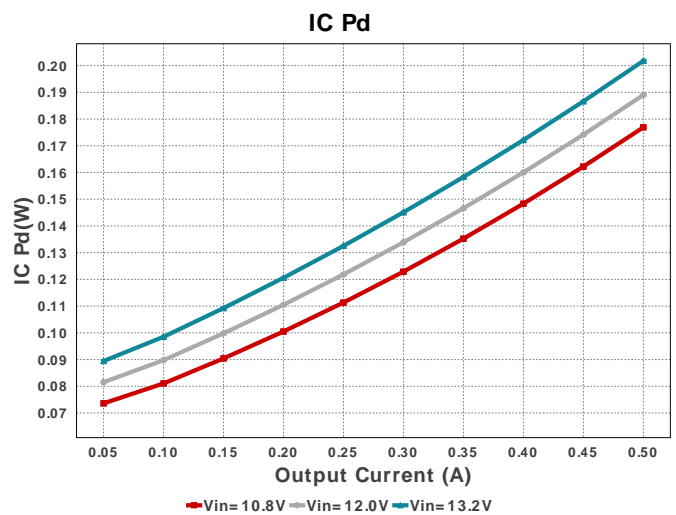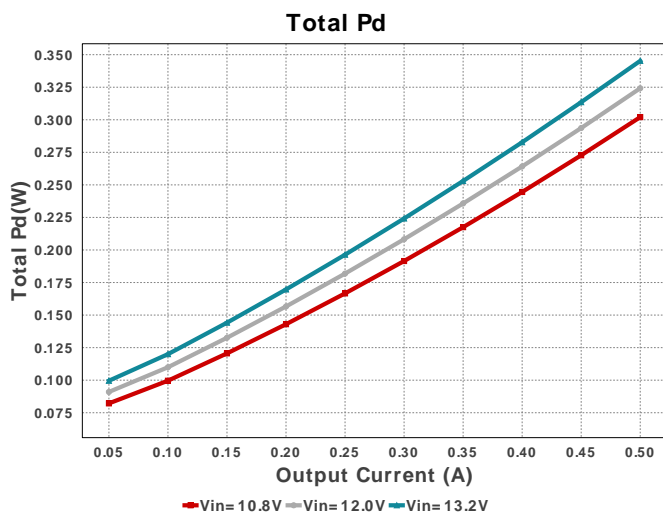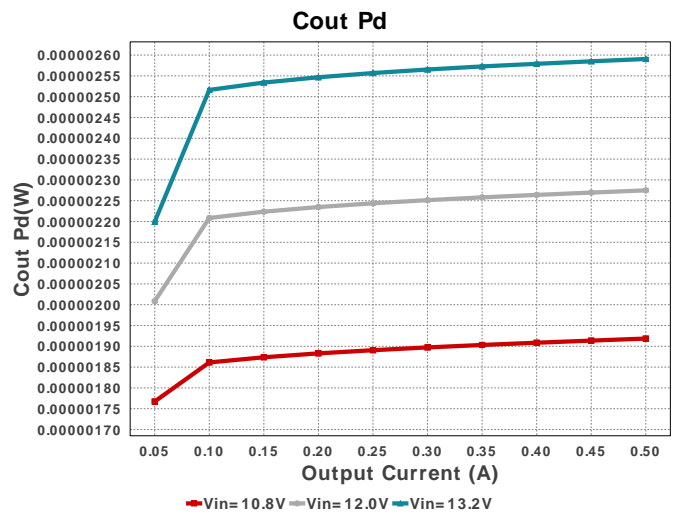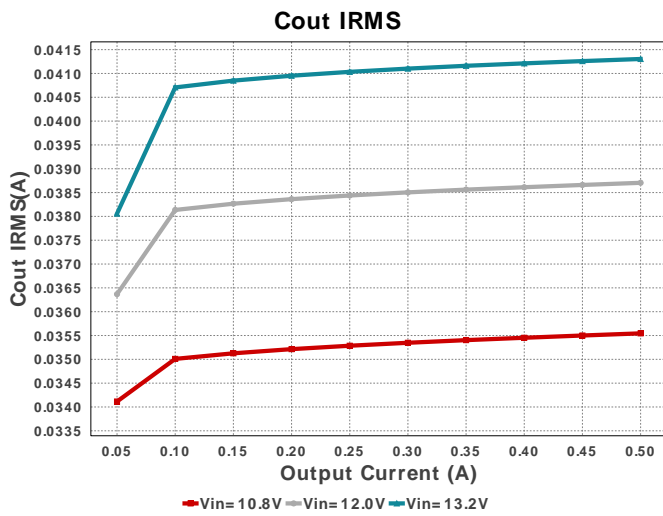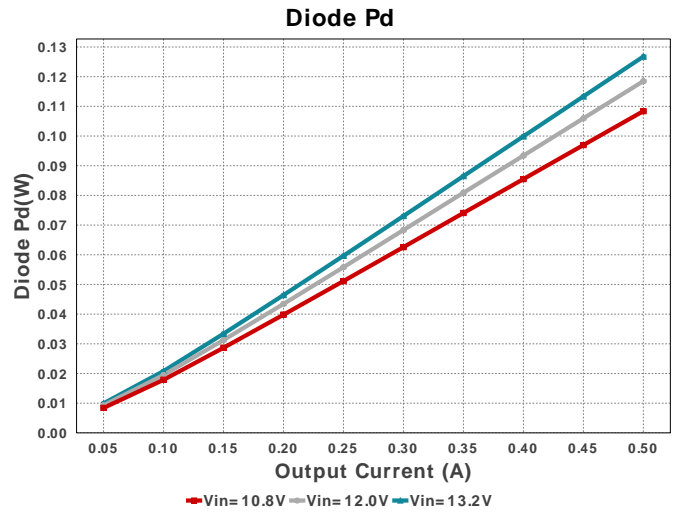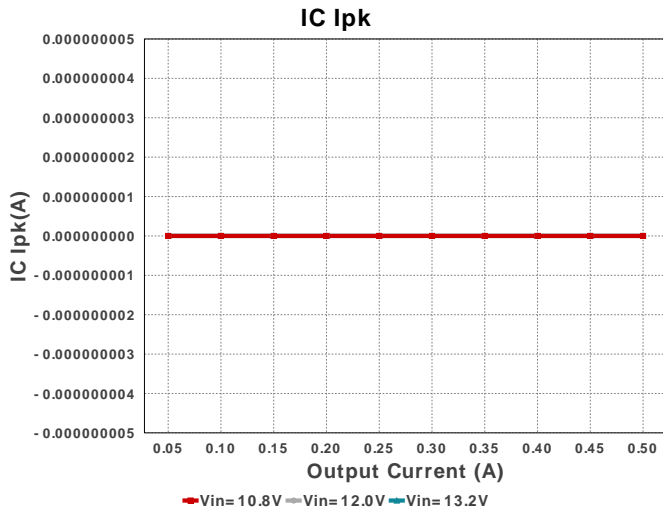

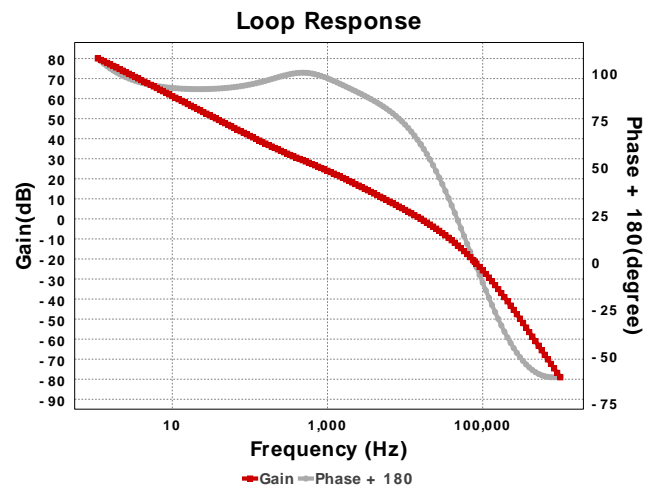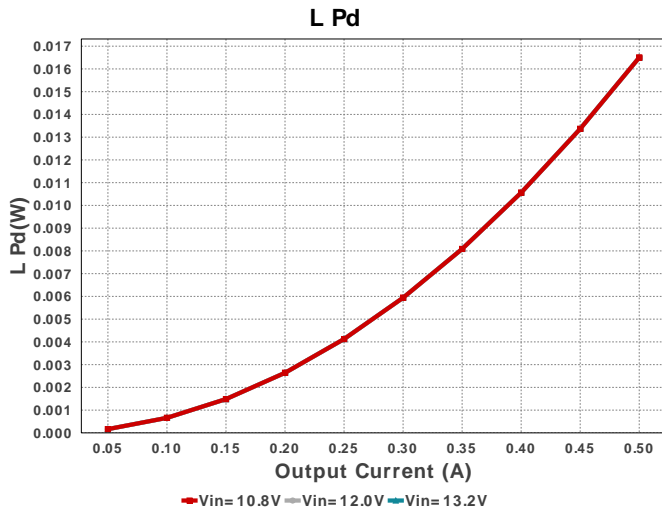

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	226.669 mA	Capacitor	Input capacitor RMS ripple current
2.	Cin Pd	190.36 μ W	Capacitor	Input capacitor power dissipation
3.	Cout IRMS	41.304 mA	Capacitor	Output capacitor RMS ripple current
4.	Cout Pd	2.591 μ W	Capacitor	Output capacitor power dissipation
5.	D1 Tj	47.749 degC	Diode	D1 junction temperature
6.	Diode Pd	126.78 mW	Diode	Diode power dissipation
7.	IC Ipk	0.0 A	IC	Peak switch current in IC
8.	IC Pd	201.78 mW	IC	IC power dissipation
9.	IC Tj	42.611 degC	IC	IC junction temperature
10.	ICThetaJA	62.5 degC/W	IC	IC junction-to-ambient thermal resistance
11.	Iin Avg	215.55 mA	IC	Average input current
12.	L Ipp	143.08 mA	Inductor	Peak-to-peak inductor ripple current
13.	L Pd	16.5 mW	Inductor	Inductor power dissipation
14.	Cin Pd	190.36 μ W	Power	Input capacitor power dissipation
15.	Cout Pd	2.591 μ W	Power	Output capacitor power dissipation
16.	Diode Pd	126.78 mW	Power	Diode power dissipation
17.	IC Pd	201.78 mW	Power	IC power dissipation
18.	L Pd	16.5 mW	Power	Inductor power dissipation
19.	Total Pd	345.244 mW	Power	Total Power Dissipation
20.	BOM Count	16	System	Total Design BOM count
Information				
21.	Cross Freq	15.937 kHz	System	Bode plot crossover frequency
Information				
22.	Duty Cycle	40.09 %	System	Duty cycle
Information				
23.	Efficiency	87.866 %	System	Steady state efficiency
Information				
24.	FootPrint	335.0 mm ²	System	Total Foot Print Area of BOM components
Information				
25.	Frequency	850.96 kHz	System	Switching frequency
Information				
26.	Gain Marg	-21.346 dB	System	Bode Plot Gain Margin
Information				
27.	Iout	500.0 mA	System	Iout operating point
Information				
28.	Low Freq Gain	80.051 dB	System	Gain at 1Hz
Information				
29.	Mode	CCM	System	Conduction Mode
Information				
30.	Phase Marg	62.581 deg	System	Bode Plot Phase Margin
Information				
31.	Pout	2.5 W	System	Total output power
Information				
32.	Total BOM	\$2.76	System	Total BOM Cost
Information				
33.	Vin	13.2 V	System	Vin operating point
Information				
34.	Vout	5.0 V	System	Operational Output Voltage
Information				
35.	Vout Actual	4.984 V	System	Vout Actual calculated based on selected voltage divider resistors
Information				

#	Name	Value	Category	Description
36.	Vout Tolerance	2.713 %	System Information	Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
37.	Vout p-p	368.596 μ V	System Information	Peak-to-peak output ripple voltage

Design Inputs

Name	Value	Description
Iout	500.0 m	Maximum Output Current
VinMax	13.2	Maximum input voltage
VinMin	10.8	Minimum input voltage
Vout	5.0	Output Voltage
base_pn	TPS54160	Base Product Number
source	DC	Input Source Type
Ta	30.0	Ambient temperature

WEBENCH® Assembly

Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of C_{in} and C_{out} , and the inductance and DC resistance of $L1$ before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

Soldering Component to Board

If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab down to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 10.8V and set the input supply's current limit to zero. With the input supply off connect up the input supply to V_{in} and GND. Connect a digital volt meter and a load if needed to set the minimum load of the design from V_{out} and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.

Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between V_{in} and GND, a load is connected between V_{out} and GND and a current meter is connected in series between V_{out} and the load. The load must be able to handle at least rated output power + 50% (7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.




WEBENCH® Electrical Simulation Report

Design Id = 5



sim_id = 1

Simulation Type = Startup

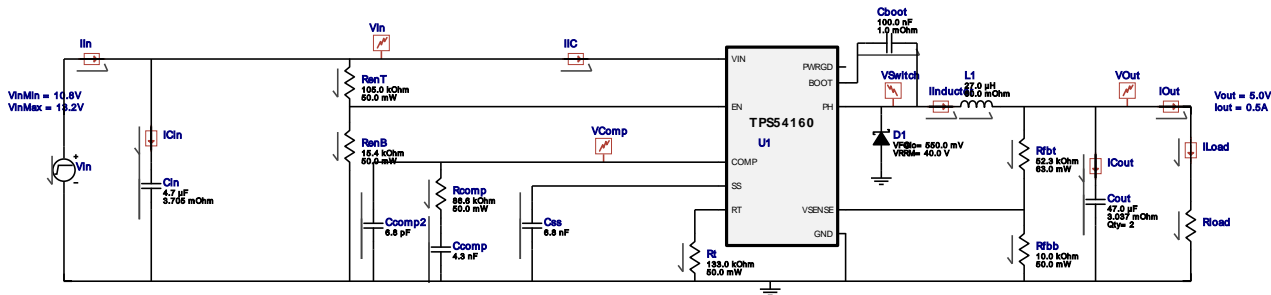

Simulation Parameters

#	Name	Parameter Name	Description	Values
1.	Rload	R	Load Resistance	10.0 Ohm

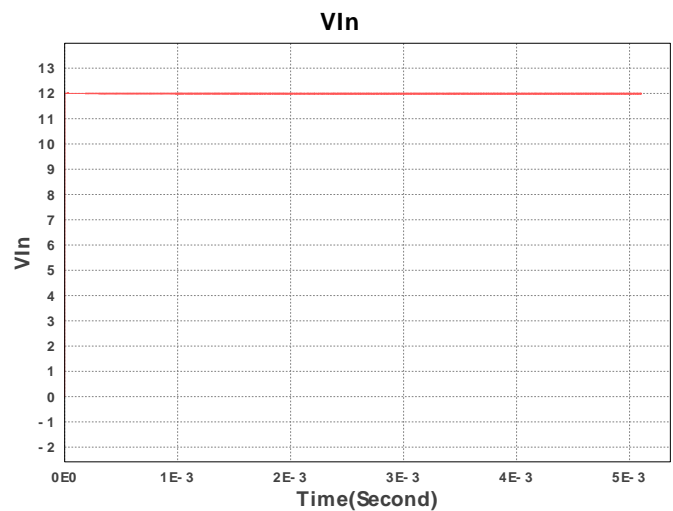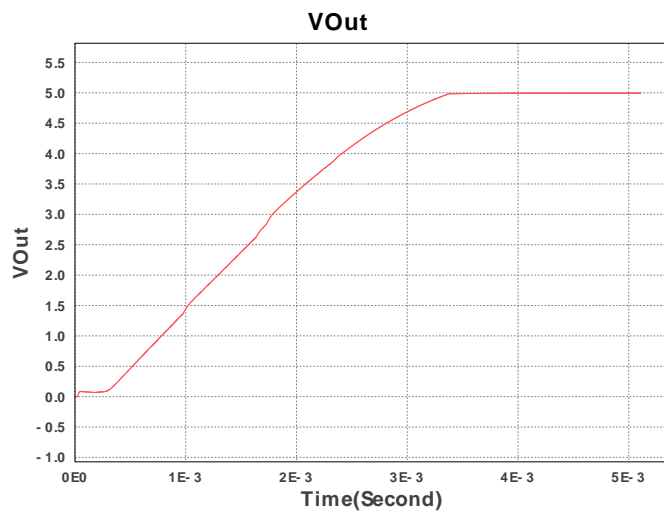

Design Assistance

1. Master key : 9401D2699F8EAF4B[v1]

2. **TPS54160** Product Folder : <http://www.ti.com/product/TPS54160> : contains the data sheet and other resources.

Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with TI products.